

Lab report

Digital Design (EDA322)

Writing Guidelines

Group TUE-PM-8

Niklas Gustafsson
Oskar Lundström

February 7, 2017

Contents

1	Introduction	1
2	Method	2
2.1	Arithmetic and Logic Unit (ALU)	2
2.2	Top-level Design	4
2.3	Controller	6
2.4	Processor's Testbench	8
2.5	ChAcc on Nexys 3 board (<i>Optional</i>)	8
2.6	Performance, Area and Power Analysis (<i>Optional</i>)	8
3	Analysis	8
A	Appendix	10

1 Introduction

(max: 1 page)

This part will introduce the reader to the report.

At the beginning, describe what the purpose of this lab report is. Then describe briefly what each section discusses and finally summarize the most important conclusions.

2 Method

2.1 Arithmetic and Logic Unit (ALU)

When we built our ALU we began by constructing the most basic component, the full-adder. We started by minimizing the boolean expression for the sum and the carry out signals using a Karnaugh diagram. We came to the conclusion that a full-adder should be built like described in the picture below.



Figure 1: A full-adder.

You can also build a full-adder using two half-adders and some extra logic. We came to this conclusion by connecting the resulting signal of the first half-adder to the second one along with the carry in signal. After this we just added the extra logic that was needed, which was an OR gate.



Figure 2: A full-adder made from two half-adders.

We created an 8-bit ripple carry adder (RCA) by connecting eight full-adders together according to the diagram below. The idea is to simply connect the carry out signal of the first full-adder to the carry in signal of the second one, and so on. The RCA was used in our original design of the ALU but later we replaced it with a carry lookahead adder (CLA).

The ALU includes a comparator unit which is used to check whether the operands are equal or not. You can implement it by using the structural or dataflow style of VHDL. We decided to do the dataflow implementation



Figure 3: A ripple carry adder.

because we thought it would be easier and that it would result in a more clean code. In order to check whether the operands are not equal we performed a bitwise XOR on the operands and OR:ed the results. This was used as the resulting NEQ signal. The EQ signal was simply an inversion of the NEQ signal.

If we were to do this in structural VHDL we would have to create a component which checked if two certain bits were not equal. We would then have to create eight such components. The input as a whole is equal if all 8 bits are equal, otherwise not.

The operation A minus B is performed by converting B to its 2-complement and then adding it with A. By passing B through 8 XOR gates, each having SUB as its second input, we can form B's 1-complement when subtracting. We connect SUB to carry-in to form the 2-complement.

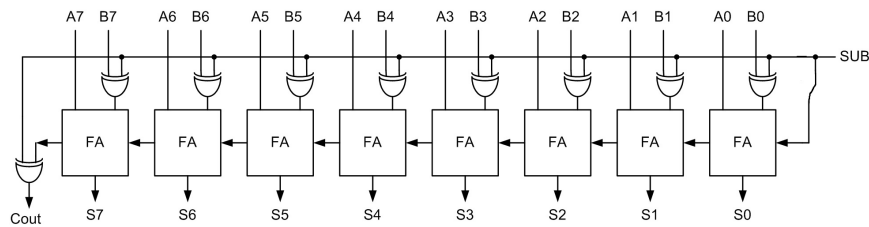


Figure 4: Logic for performing subtraction with an adder.

One thing that we learned was that in VHDL the entity names in a project have to be unique for all references to work properly.

We also learnt why the critical path for an n -bit RCA is $2n + 1$ gates. For every full adder the carry-out depth depends on the inputs (3 gates deep) and the carry-in ($2 + \text{previous depth}$). The depth is the maximum of these. For the first the depth becomes 3, for the second 5 and so on. In other words, for the first adder the inputs are the farthest away, but for the following it is the carry-in instead.

2.2 Top-level Design

Registers

We made a generic implementation of a register by letting a variable hold an integer representing the number of bits the register is able to hold. The vectors for in- and output to the register are adjusted after this variable. We implemented our register using behavioral VHDL, i.e. using a process statement, since that seemed to result in the simplest and cleanest code. Another reason for using a process statement is that we know that assigning signals values in a process statement result in flip-flops when the code is synthesized.

Memory

We also made our implementation of the memory generic. We have two integer variables, one describing the number of address bits (*addr_width*) and one describing the number of bits each memory location can hold (*data_width*). The number of bits in the input signals for address and data are adjusted after these variables. The memory itself is an array of a type which we specified. The number of entries in this type of array is 2^{addr_width} and the size of each entry is *data_width*. The read operation is asynchronous and the write operation is synchronous.

 


Figure 5: The operation of the memory.

In figure 5 interesting things happen at the red numbers.

1. The read is asynchronous, so the output is changed directly after the address is changed.
2. The write is synchronous, so the write does not happen until the positive edge.
3. When the input is changed, no write happens at the negative edge.
4. If we changed the address to something else, and then change back, the value previously written is still saved.

Bus

The bus was implemented with a mux. The 4 indata signals each had 8 bits. Bit 0 from each goes to a 4 to 1 mux, bit 1 from each to another mux and so on, i.e. the signals were muxed bitwise. The muxes are inferred by

the tools since we used a *WITH SELECT* statement. The mux select signal was created from a one-hot representation of the 4 control signals. Based on which bit was set, the corresponding mux select signal was created. If more than 1 bit are set, the bus error signal is set.

We used a multiplexer for the bus since if 2 or more control signals are set, the bus will not take an undefined value, as opposed to a tri-state version. If 0 or more than 1 control signals are set, we put 0's on the bus since we will not read from it anyway if that is the case.

Datapath

The last step was to connect all components of the datapath as described by figure 6. In the datapath entity we had signals with the same names as on that figure (made it easier to code if the names were the same). We then instantiated all components and connected them according to the figure. Some components, such as the registers, have different datatypes in different places. But since they were generic it was easy to have multiple versions.

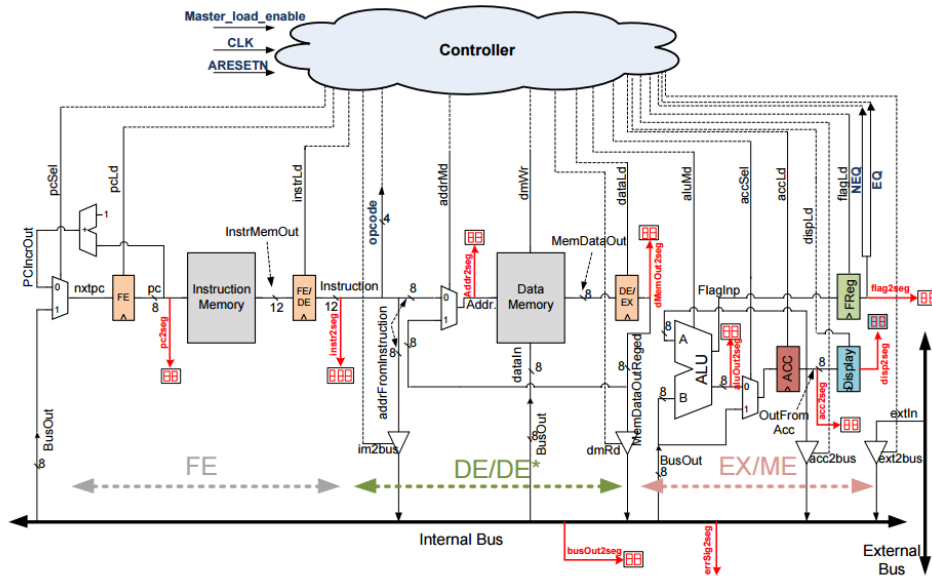


Figure 6: The datapath of the processor.

2.3 Controller

The FSM

We chose to design our controller as a Mealy FSM. We did this in order to reduce the amount of states (fewer flip-flops). If we would've chosen a Moore design we would roughly need one state for each combination of opcode and stage, although we would be able to minimize it to some extent. Fewer states means that we only have to keep track of five states, namely the stages (FE, DE, DE*, EX, ME), and hence the resulting VHDL code as well as the circuit itself becomes simpler. The statements for assigning the output signals a value are rather long. This would however be the case no matter which design we chose. If we had chosen a Moore design each row in these statements would represent a state and hence the code would be equally long.

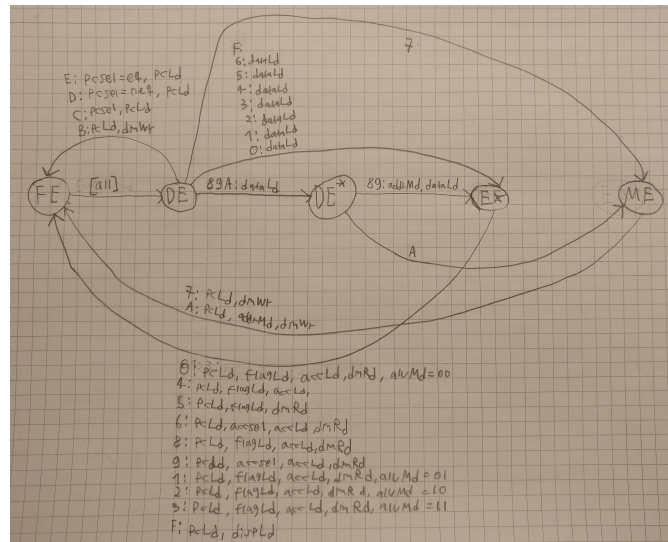


Figure 7: The state diagram.

Testing

When we first ran the testbench we noticed a problem. The contents of the data memory did not match the specifications of what it should contain after running the testbench. We started troubleshooting and found three problems.

1. We found that our EQ and NEQ signals to the controller weren't assigned at all. We fixed this but the problem remained.
2. We continued to troubleshoot the controller by examining the waveform diagram of the controller and datapath when running the test-

2.4 Processor's Testbench

(max: 2 pages)

Describe what you did in lab5. More specifically, describe how you made the testbench to verify that your processor design was functionally correct. For example, you can specify how you generated inputs to the processor during the testing, how you were reading the expected outputs and how you compare the expected outputs with the actual outputs. Also mention if your processor design was working correctly from the beginning and if not describe how you backtrack the bugs. Remember to always explain your design choices and mention any assumptions. Finally, make use of figures and tables.

2.5 ChAcc on Nexys 3 board (*Optional*)

(max: 2 pages)

Describe how you verified the correctness of your FPGA implementation. Note that the code that is executed on the implementation is the same code used for testing in Lab 5. You should compare sequences of values on various signals observed on the seven-segment displays to values seen in Modelsim simulation of the design. Please include in the report the sequence of program counter (PC) and display register values you observed during a successful execution on the FPGA.

2.6 Performance, Area and Power Analysis (*Optional*)

(max: 2 pages)

To be announced in the Lab7PM.

3 Analysis

(max: 1 page)

Summarize your results after performing all the labs (2, 3, 4 and 5).

Mention and discuss interesting findings and observations, as well as diffi-

culties in completing some of the tasks of the four last labs.

After looking at your results, draw conclusions and describe briefly the learning outcome, that is what have you learnt by performing these labs?

A Appendix

(max: 4 pages)

In the appendix, you can include extra figures or tables that don't fit in the main body of the lab report.