

# Digital design, summary, week 1


## • ASIC - Application specific integrated circuits

- Cannot change
- All the way from behavioral description to physical layout
- Expensive & time consuming fabrication
- High performance, low cost in high volumes

## • FPGA - Field programmable gate arrays

- Generic - support different hardware designs
- Behavioral description → Bitstream → loaded to FPGA
- Bought off the shelf
- low development cost

## • Levels of hardware design

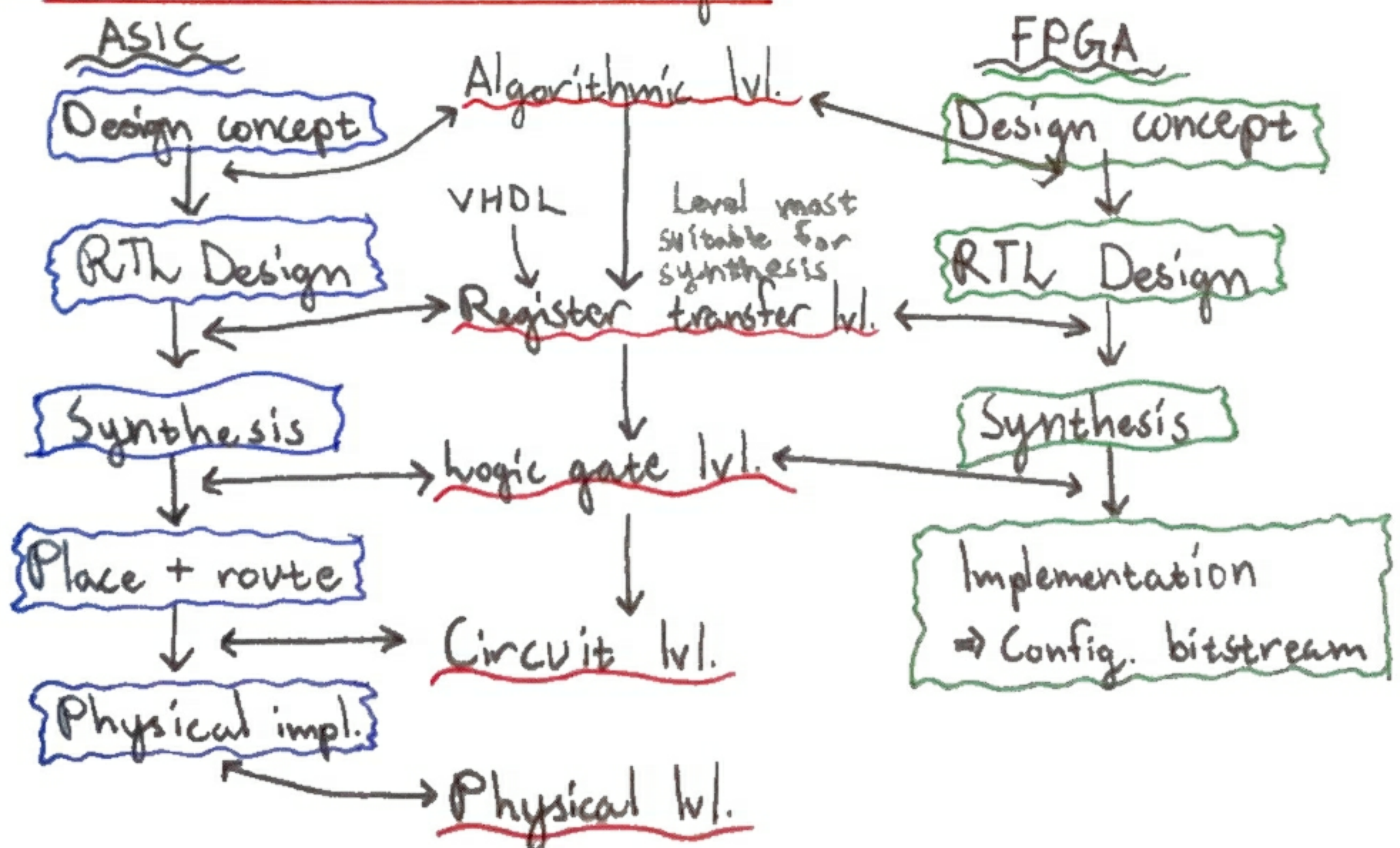



- VHDL Design styles
  - Dataflow - Boolean functions, parallel
  - Structural - Components & inter connects
  - Behavioral - More like software, sequential

### Boolean algebra

- $\overline{X \cdot Y} = \overline{X} + \overline{Y}$
- $\overline{X + Y} = \overline{X} \cdot \overline{Y}$
- $X + \overline{X} \cdot Y = X + Y$

- Associative:  $(X \cdot Y) \cdot Z = (X) \cdot (Y \cdot Z)$
- Distributive:  $X \cdot (Y + Z) = X \cdot Y + X \cdot Z$
- Commutative:  $X + Y = Y + X$

### De Morgan \*

- AND - OR  $\Leftrightarrow$  NAND - NAND
- OR - AND  $\Leftrightarrow$  NOR - NOR
- Minterm - all variables appear once, product term.  $A \cdot B \cdot \overline{C}$
- Maxterm - sum term instead.  $(A + B + \overline{C})$
- Canonical Form - all terms are minterms / all are maxterms
- $F = \sum \text{minterms} = \prod (\text{sums}) \text{ maxterms}$ ,  $F' = \prod \text{minterms} = \sum \text{max}$


### Karnaugh - diagram

- For simplification
- 1's - minterms - S.O.P
- 0's - maxterms - P.O.S

All possible:

$$F = A \cdot \overline{C} + \overline{A} \cdot C + B \cdot C + A \cdot B + \overline{A} \cdot \overline{B} \cdot \overline{D} + \overline{B} \cdot \overline{C} \cdot \overline{D}$$

 Simplest:  $F = B \cdot C + A \cdot \overline{C} + \overline{A} \cdot \overline{B} \cdot \overline{D}$ , for example





## Definition of terms

- A function  $f$  covers a function  $g$  if  $f = '1'$  when  $g = '1'$
- Implicant - A product of variables for which  $f = '1'$
- Prime implicant - An implicant that can't be covered by a more general expression
- Essential prime implicant - A prime implicant that includes a minterm which is not included by any other prime implicant.
- Edges don't line up exactly in simulation because it takes time for gates to change its output.
- Delay - Nr. of gates in a row
- Tradeoffs:
  - More area for lower delay
  - Higher delay for lower power
- Critical path - longest path from input to output
- Ripple carry adder - several full adders
- $A - B = A + B_{2x}$ . Invert all bits and add one.
- Carry select adder - keep second part of nr. in two versions ( $C_{in} = 0$  and  $C_{in} = 1$ )
- Carry look-ahead adders
  - A carry can either be generated or propagate through
  - Generated if  $A = 1$  &  $B = 1$ .  $g_i = a_i \cdot b_i$
  - Propagates if either  $A$  or  $B = 1 \Rightarrow p_i = a_i \oplus b_i$
  - $C_{in+i+1} = g_i + p_i \cdot C_{in+i}$ ,  $S_i = p_i \oplus C_{in+i} = (a_i \cdot b_i) \oplus C_{in+i}$
- Gives us logarithmic time complexity



## Chalmers accumulator processor - ChAcc

- Accumulator - Keeps result of most recent operation
- Simple but slow - ~2-4 clock cycles per instruction
- Operates on 8-bit data
- Datapath - where data flow
  - Used / modified
  - Read / written from / to memory
  - Memory, registers, ALU
- Controller - synchronizes processor's components and orchestrates operations
- Communications bus - Transfers data
- Harvard architecture - separate memory for instructions and data. 8-bit addresses.
- 4-bit opcode and 8-bit argument
- Controller breaks datapath into five stages
  - Fetch, decode, decode\*, execute, memory
  - Instructions doesn't pass through all stages
- Controller is a finite state machine